

A (Printed Pages 4)  
(20622) Roll No.  
BCA-II Sem.

**18007**

**B.C.A. Examination, June-2022**

**DIGITAL ELECTRONICS AND  
COMPUTER ORGANISATION**

**(BCA-204)**

*Time : Three Hours /* *[Maximum Marks : 75]*

**Note :** Attempt **all** the Sections as per instructions.

**Section-A**

**(Very Short Answer Questions)**

**Note :** Attempt **all five** questions. Each question carries 3 marks. Very short answer is required not exceeding 75 words.

1. Write Demorgan's Laws. 3
2. Differentiate between flip flop and latches. 3

3. Differentiate between combinational logic circuit and sequential circuits. 3
4. Construct half subtractor using logic gates. 3
5. Draw the memory hierarchy structure and mark the arrow from low to high (Speed) & high to low (Cost). 3

**Section-B**

**(Short Answer Questions)**

**Note :** Attempt any **two** questions.

6. Minimize the following Boolean function using K-map-. 7½  
$$F(A,B,C,D) = \sum (3,4,5,7,9,13,14,15)$$
7. (i) Convert the SR flip flop to JK flip flop draw the truth table of JK flip flop also. 5  
(ii) Implement 4:1 multiplexer using 2:1 multiplexer 2½

**P.T.O.**

**18007/2**

8. (i) simplify the expression: 4

$$F(A,B,C,D) = ACD + \bar{A}B + \bar{D} \text{ by K-map.}$$

(ii) How many flip flops are needed to implement a 32 bit register. 3½

### Section-C

#### (Detailed Answer Questions)

**Note :** Attempt any **three** questions.

9. (i) Which gates are called universal gates and why? 5

(ii) Draw a full subtractor circuit using NAND gate. 10

10. What do you mean by shift register? What is the need of shift register? Draw & explain bidirectional shift register. 15

11. Draw and explain 4-bit binary synchronous counter. 15

12. (i) Differentiate between EPROM & EEPROM. 5

(ii) Differentiate between SRAM & DRAM. 5

(iii) Differentiate between L<sub>1</sub> cache & L<sub>2</sub> cache. 5

13. (i) Differentiate between ROM & PROM. 3

(ii) Describe USB. 3

(iii) Differentiate between primary memory and secondary memory. Also list the examples of primary memory and secondary memory. 3

(iv) Explain the concept of Virtual memory. 3

(v) Draw basic cell of memory. 3

18007/3

P.T.O.

18007/4